

## Bipolar Junction Transistors

### Introduction

PHY2003 does not require a knowledge of the semiconductor physics underlying *how* transistors work, they are treated as nonlinear three-terminal devices. Figure 1 defines the current conventions used in PHY2003. The rules-of-thumb for analysing bipolar junction transistor (BJT) circuits at low-frequencies are:

$$\begin{aligned} \text{NPN: } & V_C > V_B = V_E + 0.6 \text{ V} \\ \text{PNP: } & V_C < V_B = V_E - 0.6 \text{ V} \end{aligned} \quad (9.1)$$

$$\text{if } \begin{cases} \text{NPN: } V_B < V_E + 0.6 \text{ V} \\ \text{PNP: } V_B > V_E - 0.6 \text{ V} \end{cases} \text{ then } I_C = 0 \text{ else } I_C = h_{FE} I_B \quad (9.2)$$

$$\text{typically } 50 < h_{FE} < 500 \text{ therefore } I_E \approx -I_C. \quad (9.3)$$

### Required Reading

Bipolar Transistors – Storey (1998) §7.1–7.7 pp. 234–295 / (2006) §8.1–8.8 pp. 221–284.

Another source of the required information are the WWW references listed under:

<<http://newton.ex.ac.uk/teaching/CDHW/Electronics2/ElectronicsResources.html#xistors>>



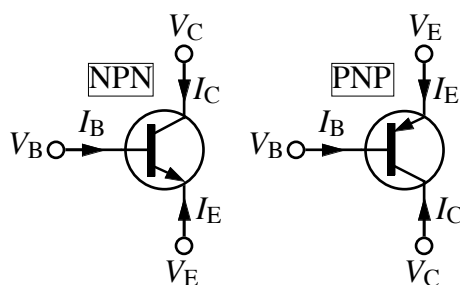


Figure 9.1 Current conventions

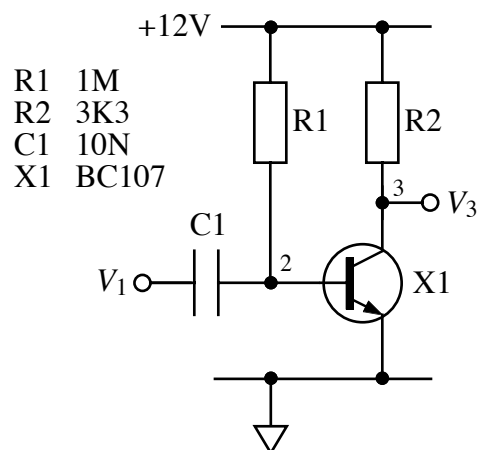

Circuit 9.1 Common Emitter Amplifier

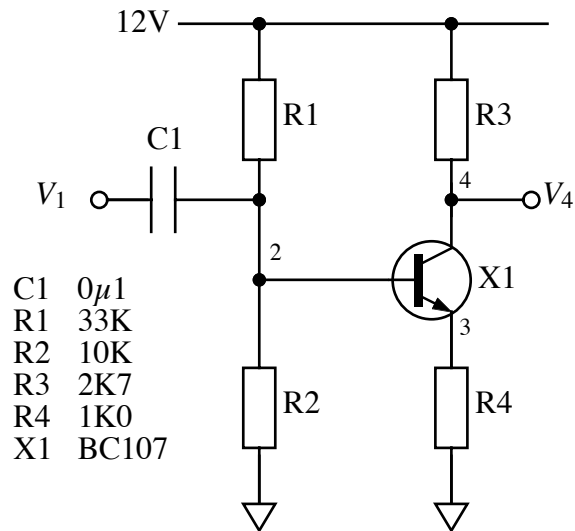

Circuit 9.2 Series Feedback Amplifier

Exercise 9.1 Analyse circuit 9.1 using typical values from the BC107 datasheet and find:

- the quiescent voltage at node 3,
- the DC impedance of node 2 and hence the low-frequency  $-3$  dB point
- the small-signal voltage gain  $v_3/v_1$  at 1 kHz and 10 kHz.

Answers: (a) 6.4 V (assuming HFE = 150) (b) 2.2 k $\Omega$ , 7.2 kHz (c)  $-60$  and  $-400$

Exercise 9.2 Analyse circuit 9.2 using typical values from the BC107 datasheet and find:

- the quiescent voltage at node 3
- the quiescent voltage at node 4
- the small-signal gain  $v_4/v_1$  at 1 kHz

Answers: (a) 2.1 V (b) 6.3 V (c)  $-60$  and  $-400$  (c)  $v_4/v_1 = -2.7$